

Solution Key 3 - SH2025

- S.M.

2M

J 2M



$$I_2 = 2 \text{ A.}$$

3M.

1

3M

$-2M$

$-2M$

Working principle of BJT - 3M.

Q. 2 A) $\phi = 37^\circ$

$$Z_{coil} = \frac{V_{coil}}{I} = \frac{171}{3} = 57 \Omega$$

$$Z = V/I = 240/3 = 80 \Omega$$

$$(Pf)_{ckt} = \frac{R+r}{Z}$$

$$R+r = (\cos 37^\circ \times 80) = 63.89 \Omega \quad \text{--- } 2M$$

$$Z = \sqrt{(R+r)^2 + X_L^2}$$

$$Z^2 = (R+r)^2 + X_L^2$$

$$\boxed{X_L = 48.15 \Omega}$$






$$Z_{coil} = \sqrt{r^2 + X_L^2}$$

$$\boxed{r = 30.51 \Omega}$$

$$r + R = 63.89$$

$$\boxed{R = 33.38 \Omega}$$

Q. 2 B) Find R_{xy}

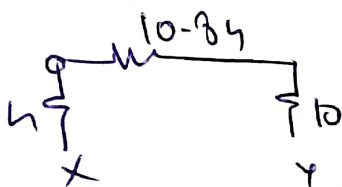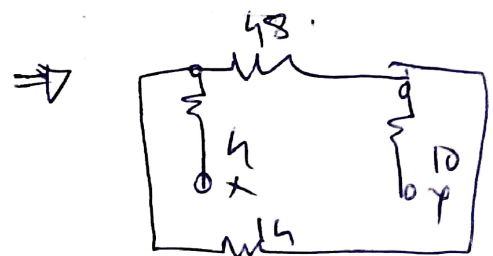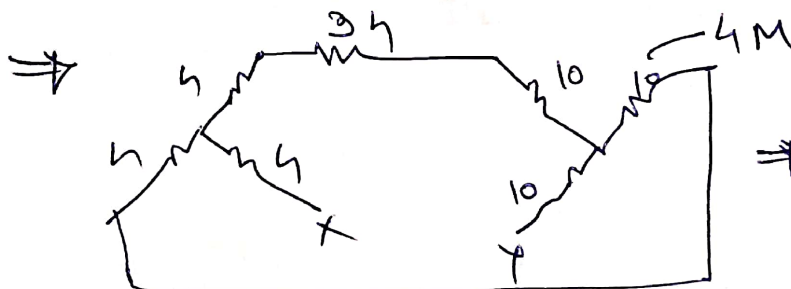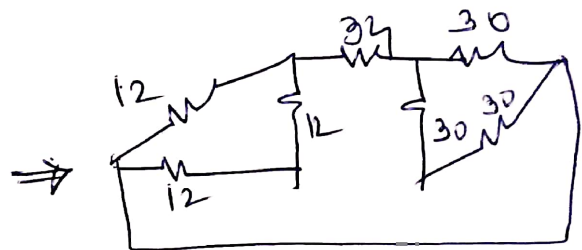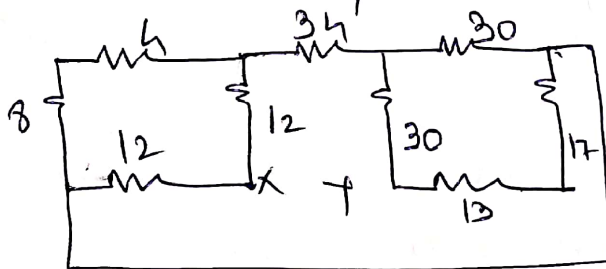

$$R_{xy} = 24.84 \Omega$$



RMS value derivation — 3M.

sk 3-2

Q. 2 c) $i = 14.14 \sin 377t$

$$I_m = 14.14 \text{ A} \quad \text{— 1M}$$

i) $I_{rms} = I_m / \sqrt{2} = 9.99 \text{ A}$

$$\omega = 2\pi f$$

$$377 = 2\pi f$$

ii) $f = 60.03 \text{ Hz}$ — 1A

iii) $T = \frac{1}{f} = \frac{1}{60} = 0.0166 \text{ sec.}$

$$t = 3 \times 10^{-3}$$

$$i = 14.14 \sin 377 \times 3 \times 10^{-3}$$
$$= 14.14 \sin \left[377 \times 3 \times 10^{-3} \times \frac{180}{\pi} \right]^\circ \quad \text{2M}$$

$$= 14.14 \sin 64.83$$

$$i = 12.86 \text{ A}$$

iv)

$$10 = I_m \sin 377t$$

$$10 = 14.14 \sin 377t$$

$$\sin 377t = 0.707 \quad \text{— 3M}$$


$$\sin \left(377t \times \frac{180}{\pi} \right) = 0.707$$

$$377t \times \frac{180}{\pi} = \sin^{-1} 0.707 = 0.7852$$

$$t = \frac{2.4656}{377 \times 180} = 3.6 \times 10^{-5} \text{ sec.}$$


$$t = 2.083 \text{ ms}$$

(02D)

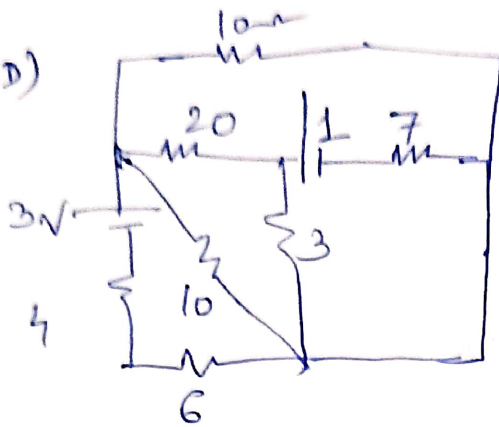


I_{20}

$\Rightarrow R_{Th} =$

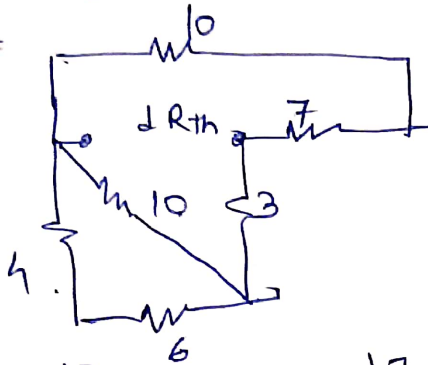


$\Rightarrow$

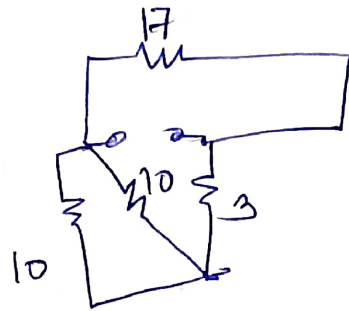


— 3M

$\Rightarrow$

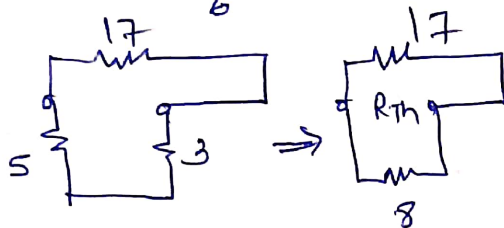

$R_{Th} = 5.44 \Omega$

$\Rightarrow V_{Th},$

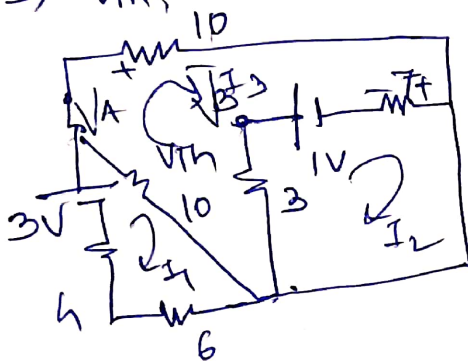

$$-20I_1 + 10I_3 = -3 \quad (1)$$

$$0I_1 - 10I_2 + 10I_3 = 1 \quad (2)$$

$$10I_1 + 10I_2 - 30I_3 = -1 \quad (3)$$

$$I_1 = 0.2A, I_2 = 0, I_3 = 0.1$$

$$V_{Th} = -1 + 0 + 10I_3 = -1 + 10 \times 0.1 = 0$$

— 4M

$$V_{Th} = V_A - V_B = 0.7V$$

$$V_A \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{10} \right) = \frac{3}{10}$$

$$V_A = 1V$$

$$V_B \left(\frac{1}{3} + \frac{1}{7} \right) = \frac{1}{7}$$

$$V_B = 0.1428$$

$$V_B = 0.3V$$

Thevenin



$$I_L = V_{Th} / (R_{Th} + R_L)$$

$$= 0.0275A$$

Q.2 E) $R = V_R / I = 125 / 5 = 25 \Omega$

i) $Z_{coil} = \frac{200}{5} = 40 \Omega$

$Z = V / I = 50 \Omega$

— 1M

$Z_{coil} = \sqrt{r^2 + X_L^2}$

$40^2 = r^2 + X_L^2$ — (1)

$Z = \sqrt{(R+r)^2 + X_L^2}$

$50^2 = (R+r)^2 + X_L^2$ — (2)

— 2M

Solve eqn (1) & (2)


$r = 5.5 \Omega$

— 2M

$X_L = 39.62 \Omega$

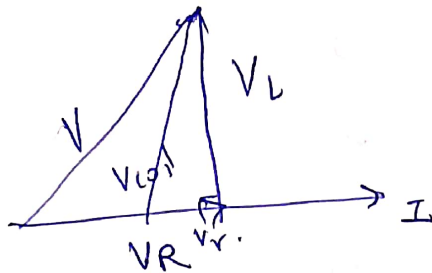ii) $P_{coil} = I^2 r = 5^2 \times 5.5 = 137.5 W$ — 2M

$PF(coil) = r / Z_{coil} = 0.137$ lagging



— 3M

Q.3 A)

$I \times 15 = 30$

— 1M

$I = 2 A$

$I_{sc} = 7 A$

— 1M

$-(7 \times 5) - IR + 100 - 30 = 0$

— 3M

$R = 17.5 \Omega$

B) Derivation of emf equation — 5M.

C) Working — 5M
with diagram

D) Working of 3 ϕ Induction motor with,
diagram — 5M.