

Subject: BEEE

Sk2 - ①

Subject code: - FEE103

Solution key 2: - SH2025

Q.1 A) Thevenin Theorem statement - 3M

Example - 2M


Q.1 B) Construction - 2M

Working principle - 2M

Application of zener diode - 1M.

Q.1 C) Comparison of core type and shell type. At least 7^{to} 8 points should be discussed.

Q.1 D)

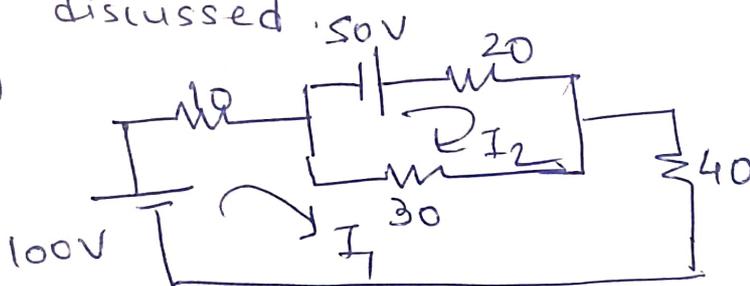

$$\Rightarrow \begin{cases} -80I_1 + 30I_2 = -100 & \text{①} \\ 30I_1 - 50I_2 = -50 & \text{②} \end{cases} \quad \left. \vphantom{\begin{matrix} ① \\ ② \end{matrix}} \right\} 4M$$

$$I_1 = 2.096 \text{ A}$$

$$I_2 = 2.25 \text{ A}$$

$$\therefore \boxed{I_{20\Omega} = 2.25 \text{ A}}$$

- 1M.

Q.2 A) Construction with diagram - 5M.

Working principle - 5M.

(Q 2 B) For coil A

PF = 0.8

$\phi_A = 36.87^\circ$

$Z_A = 10/2 = 5 \Omega$

$\frac{r_A}{Z_A} = 0.8$

$r_A = 4 \Omega$

- 3M

$Z_A = \sqrt{r_A^2 + x_A^2}$

$x_A = 3 \Omega$

For coil B.

PF = 0.7

$\phi_B = 45.57^\circ$

$Z_B = 5/2 = 2.5$

$r_B/Z_B = 0.7$

$r_B = 1.75$

- 3M

$Z_B = \sqrt{r_B^2 + x_B^2}$

$x_B = 1.79 \Omega$

Total Impedance with A & B coil.

$Z = \sqrt{(r_A + r_B)^2 + (x_A + x_B)^2}$

$Z = 7.48 \Omega$

- 2M


$V = I \cdot Z = 14.96 \text{ V}$

(PF) ckt = $\frac{r_A + r_B}{Z} = \frac{4 + 1.75}{7.48}$


= 0.77 lagging.

- 2M

(Q 2 C) For Rth

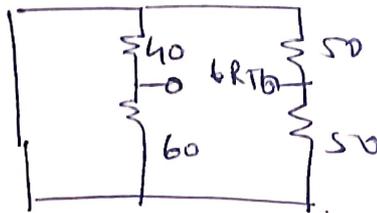


$\frac{40 \times 60}{100} = 24 \Omega$

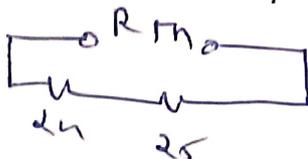

$R_{th} = 49 \Omega$

$\frac{50 \times 50}{100} = 25 \Omega$

= For Vth

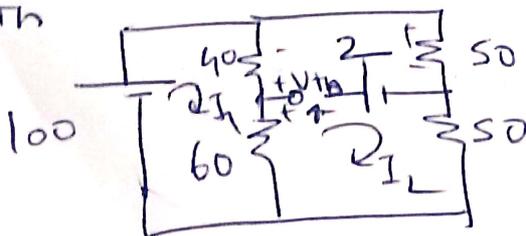

$-100 I_1 + 100 I_2 = -100$

$100 I_1 - 200 I_2 = 0$

$I_1 = 2 \text{ A}, I_2 = 1 \text{ A}$

$-V_{th} - 2 + 50 I_2 + 40(I_2 - I_1) = 0$

$$V_{in} = -2 + 50 \times 1 + 40(1-2)$$

$$= -2 + 50 - 40$$

$$= 8V$$

— 4M

$$P_{max} = V_{in}^2 / 4R_{in} = 64 / 4 \times 49 = 0.326 \text{ Watts}$$

— 3M

(2D) for star $I_L = I_{ph}$
 $V_L = \sqrt{3} V_{ph}$

$$Z_{ph} = R_{ph} + jX_{ph}$$

$$V_L = 440V, f = 50 \text{ Hz}, P = 1.5 \text{ kw}$$

$$V_{ph} = \frac{440}{\sqrt{3}} = 254.03V$$

— 2M

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$I_L = 9.84A = I_{ph}$$

— 3M

$$Z_{ph} = V_{ph} / I_{ph} = 25.82 \Omega$$

— 1M

$$\phi = 78.46^\circ$$

— 1M



$$Z_{ph} = 25.82 \angle 78.26^\circ = 5.17 + j25.3 \Omega$$






$$R = 5.17 \Omega$$

$$X_L = 25.3$$

$$L = 0.08 \text{ H}$$

} 3M

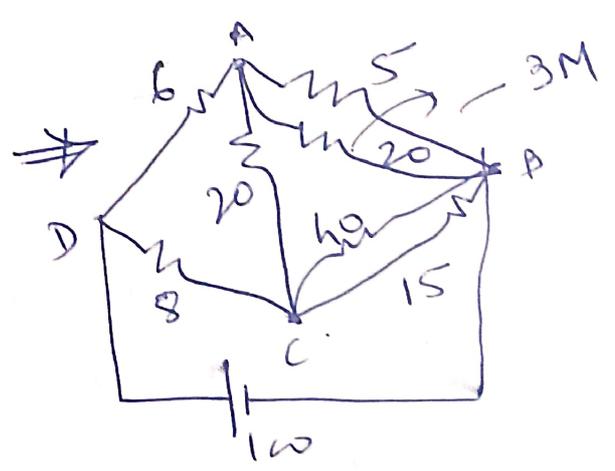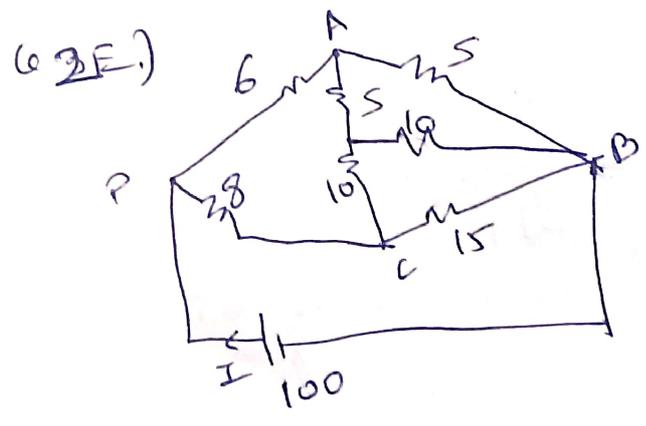

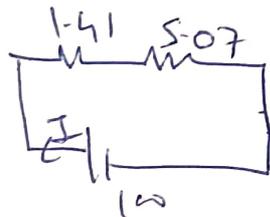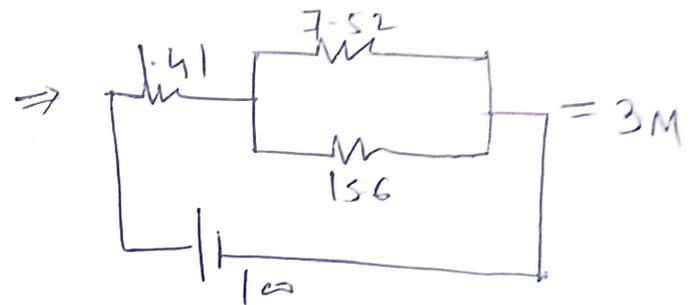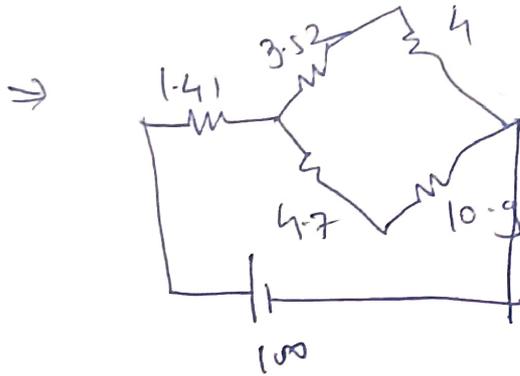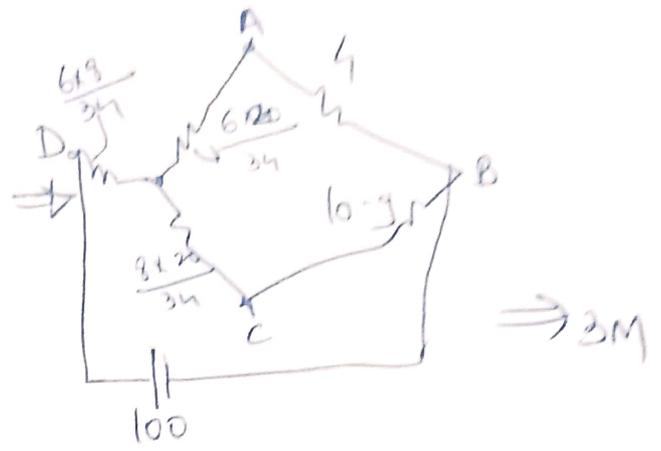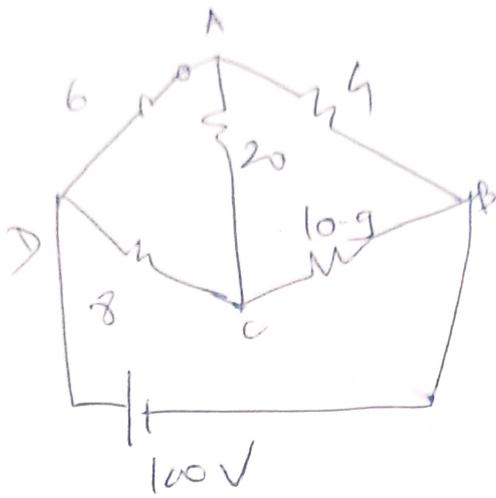

$$I = \frac{100}{1.41 + 5.07} = \underline{\underline{15.4 \text{ A}}} - \underline{\underline{1M}}$$

Q 3A) Derivation - RMS value - SM.
 $I_{rms} = 0.707 I_m$

Q 3B). Two losses - Core or Iron
 Copper & winding in details - SM

Q 3C) $P_{\Delta} = 3 P_{star} - 3M$.

$$P = \sqrt{3} V_L I_L \cos \phi \underline{\underline{W}}, \quad Q = \sqrt{3} V_L I_L \sin \phi \underline{\underline{VAR}}$$

$$S = \sqrt{3} V_L I_L \underline{\underline{VA}} - 2M$$

Q 3D) Compare FET with BJT
 - compare atleast 6 to 7 points of comparison - SM.