

Branch : All

course: BEEE

Year / Semester : FE / I

course code : FEC 103

Time : 2 Hrs.

Marks : 60

Solution / Marking scheme for QP. 4

Q.1 a) Losses in Transformer 2 Marks
 Types - 3 Marks
 Definition/Explanation -

b) Application of BJT as an amplifier

Diagram - 2 Marks

Explanation - 3 Marks

c) Three phase induction motors are of self starting type.

Figure - 2 Marks

Explanation/Justification - 3 Marks

d) Solⁿ :-

i) $i = I_m \sin \omega t = 10 \sin 2\pi \times 50 t = 10 \sin 314 t$ (1M)

ii) Value of current after $\frac{1}{360}$ second,

$$\begin{aligned} i &= 10 \sin 314 t \\ &= 10 \sin 314 \left(\frac{1}{360} \right) \\ &= 10 \sin \left(0.873 \times \frac{180^\circ}{\pi} \right) \\ &= 10 \sin 50^\circ \end{aligned}$$

$$i = 7.67 \text{ A} \quad (2M)$$

iii) Time taken to reach 7.67 A for the first time

$$i = I_m \sin 314 t$$

$$7.67 = 10 \sin 314 t$$

$$\sin 314 t = 0.767$$



$$\sin \left(314 t \times \frac{180^\circ}{\pi} \right) = 0.767$$

$$\begin{aligned} 314 t \times \frac{180}{\pi} &= \sin^{-1} 0.767 \\ &= 50.08 \end{aligned}$$

$$t = 2.78 \text{ ms}$$

(2M)

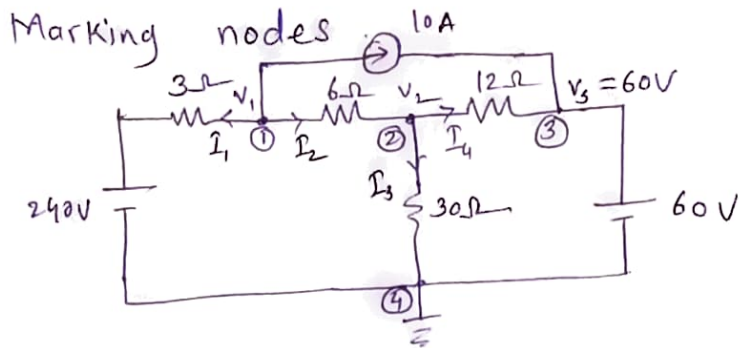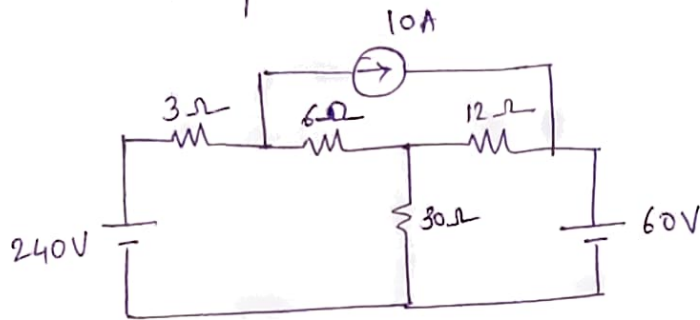Q. 2 A) Find current through 6Ω resistance using Nodal Analysis.



(2 m)

KCL at node 1,

$$I_1 + I_2 + 10 = 0$$

$$\frac{V_1 - 240}{3} + \frac{V_1 - V_2}{6} + 10 = 0$$

$$3V_1 - V_2 = 420 \quad \text{--- (1)} \quad (2 m)$$

KCL at node 2,

$$I_2 = I_3 + I_4$$

$$\frac{V_1 - V_2}{6} = \frac{V_2 - 0}{30} + \frac{V_2 - 60}{12}$$

$$60V_1 - 102V_2 = -1800 \quad \text{--- (2)} \quad (2 m)$$

solving eqⁿ (1) & (2)

$$V_1 = 181.46 \text{ V}$$

$$V_2 = 124.39 \text{ V}$$

(2 m)

$$\therefore I_{6\Omega} = \frac{V_1 - V_2}{6} = \frac{181.46 - 124.39}{6} = 9.51 \text{ A.}$$

(2 m)

Q. 2 B) solution :-

(2)

a) Star connection :

Let impedance of each coil is Z_{ph} ,

Resistance of each coil, $R_{ph} = 20 \Omega$

Inductance of each coil, $L = 0.5 H$

Reactance of each coil, $X_L = 2\pi fL = 2\pi \times 50 \times 0.5$
 $= 157 \Omega$ (1M)

Rectangular form of Z_{ph} , $\bar{Z}_{ph} = (20 + j157) \Omega$ (1M)

Polar form of Z_{ph} , $\bar{Z}_{ph} = (158.27 \angle 82.74) \Omega$

$\therefore Z_{ph} = 158.27 \Omega$ & $\phi = 82.74^\circ$ (1M)

Phase voltage, $V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 V$ (1M)

Phase current, $I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{158.27} = 1.46 A$ (1M)

$I_L = I_{ph}$

$\therefore I_L = 1.46 A$ (1M)

Total power absorbed, $P = \sqrt{3} V_L \times I_L \cos \phi$
 $= \sqrt{3} \times 400 \times 1.46 \times \cos 82.74^\circ$
 $= 127.83 W$ (1M)

b) Delta connection :

$\bar{Z}_{ph} = (158.27 \angle 82.74) \Omega$


$V_L = V_{ph} = 400 V$

$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{158.27} = 2.53 A$ (1M)


$I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 2.53 = 4.38 A$ (1M)

Total power absorbed, $P = \sqrt{3} V_L I_L \cos \phi$
 $= \sqrt{3} \times 400 \times 4.38 \times \cos 82.74^\circ$
 $P = 383.48 \text{ W} \quad (1 \text{ m})$

Q. 2 c)

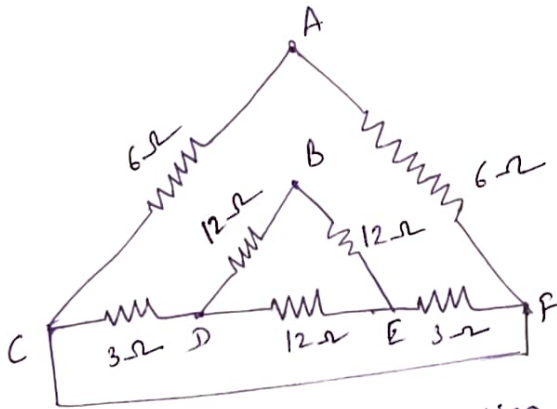

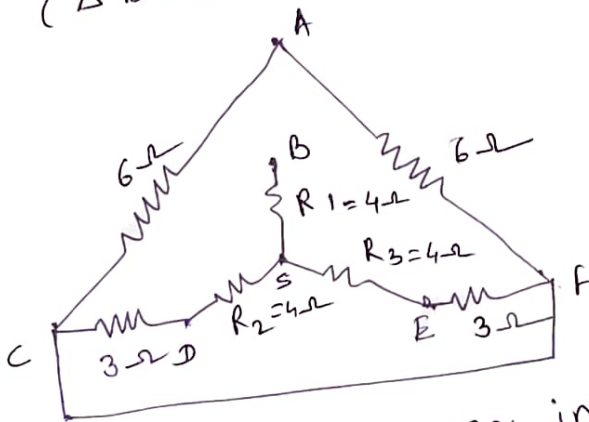
Solⁿ: - Converting delta connection formed by three 12Ω resistors (ΔBDE) into eqt star connection.



$$R_1 = R_2 = R_3 = \frac{12 \times 12}{12 + 12 + 12} = 4 \Omega$$


(2 m)

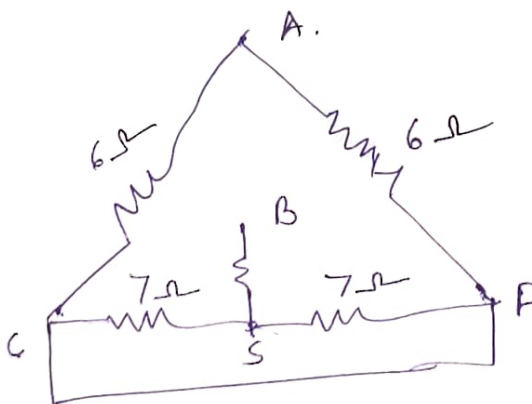In branch CDS, 3 & 4Ω are in series. Also in branch SEF, 4 & 3Ω are in series.




(2 m)

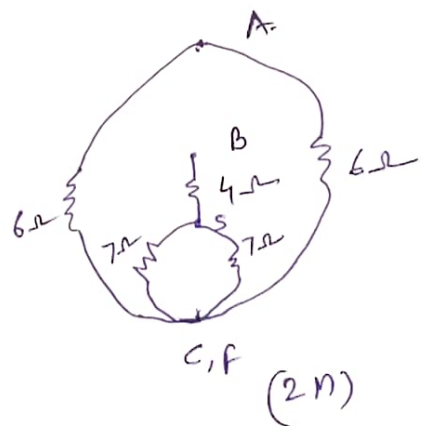Node C & F are same. \therefore Joining them.




(2 m)

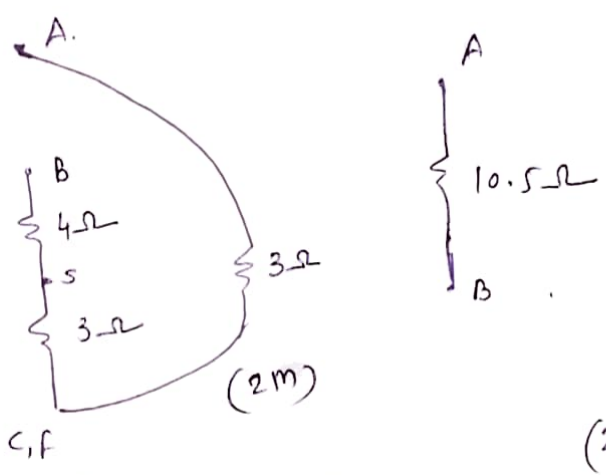


$\therefore R_{eq} = R_{AB} = 10.5\Omega$

Q.2 d)

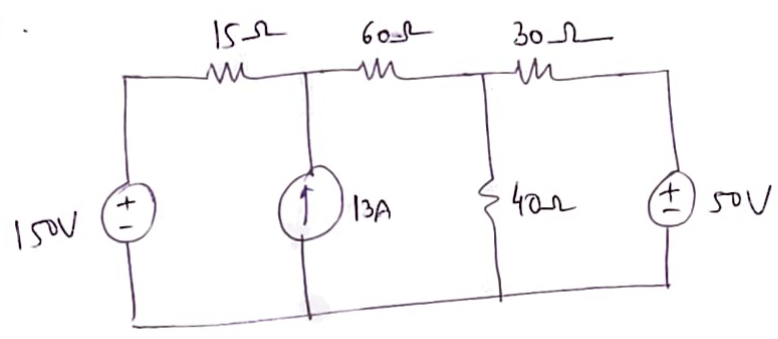


Marking R_L

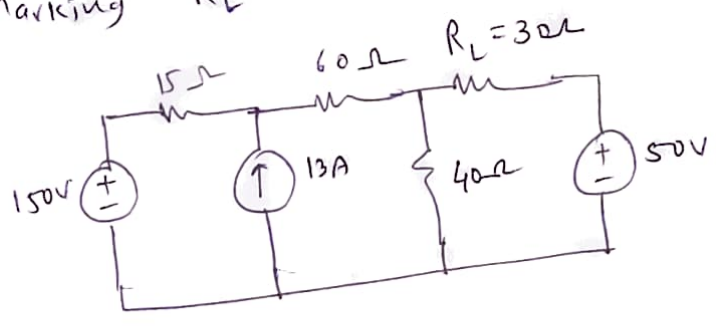

(1m)

V_{Th} calculation: -

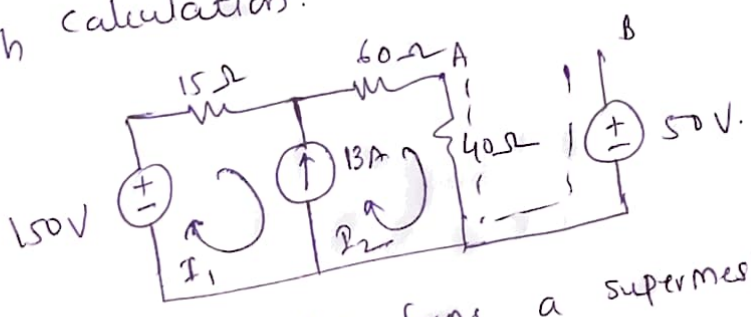

(2m)

Mesh 1 & 2 forms a supermesh

$I_2 - I_1 = 13$ — (1)

$-15I_1 - 60I_2 - 40I_2 + 150 = 0$

$-15I_1 - 100I_2 = -150$ — (2)

(2m)


solving eqⁿ (i) & (ii)

$$I_2 = 3A$$

$$\begin{aligned} \therefore V_{Th} &= V_{AB} \\ &= -50 + 40 I_2 \\ &= -50 + 40 \times 3 \\ &= 70V \end{aligned}$$

(1M)

2) R_{Th} calculation:

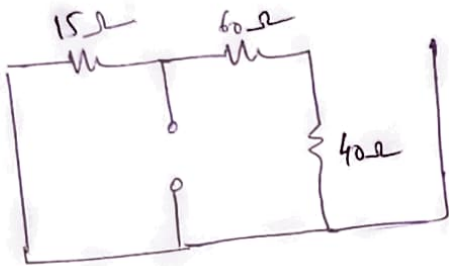


$$\therefore R_{Th} = R_{AB} = 26.09 \Omega$$

(2M)

$$3) I_L = \frac{V_{Th}}{R_L + R_{Th}}$$

$$I_L = I_{30\Omega} = \frac{70}{30 + 26.09} = 1.248 A \text{ (} \rightarrow \text{)} \quad (2M)$$

Q. 2 E)

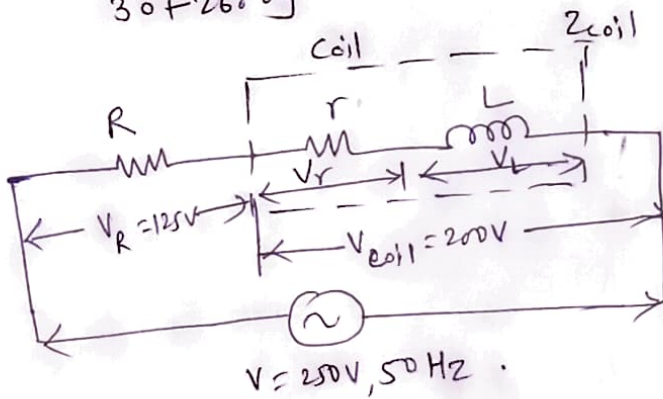

$$V = 250V, 50 \text{ Hz}$$

$$i) \text{ Resistance } R = \frac{V_R}{I} = \frac{125}{5} = 25 \Omega \quad (1M)$$

$$\text{Impedance of the coil, } Z_{coil} = \frac{V_{coil}}{I} = \frac{200}{5} = 40 \Omega \quad (1M)$$

$$\text{Total impedance of the circuit, } Z = \frac{V}{I} = \frac{250}{5} = 50 \Omega \quad (1M)$$

$$Z_{\text{coil}} = \sqrt{r^2 + X_L^2}$$

$$Z_{\text{coil}}^2 = r^2 + X_L^2$$

$$(40)^2 = r^2 + X_L^2 \quad - \textcircled{1}$$

Also, $Z = \sqrt{(R+r)^2 + X_L^2}$

$$Z^2 = (R+r)^2 + X_L^2$$

$$(50)^2 = (25+r)^2 + X_L^2 \quad - \textcircled{2} \quad (2M)$$

from eqⁿ $\textcircled{1}$ & $\textcircled{2}$

$$r = 5.5 \Omega$$

$$X_L = 39.62 \Omega$$

ii) Power absorbed $P_{\text{coil}} = I^2 r = (5)^2 \times 5.5 = 137.5 \text{ W}$ (2M)
(1M)

iii) $(\text{PF})_{\text{coil}} = \frac{r}{Z_{\text{coil}}} = \frac{5.5}{40} = 0.137$ lagging (1M)

iv) Phasor diagram,

Take 'I' as reference phasor,

$$\text{eq}^n \quad \bar{V} = \bar{V}_R + \bar{V}_{\text{coil}}$$


$$\bar{V} = \bar{V}_R + \bar{V}_r + \bar{V}_L$$

$$V_R = 125 \text{ V}$$

$$V_r = I r = 27.5 \text{ V}$$





$$V_L = I X_L = 198.1 \text{ V}$$

Scale $1 \text{ cm} = 25 \text{ V}$

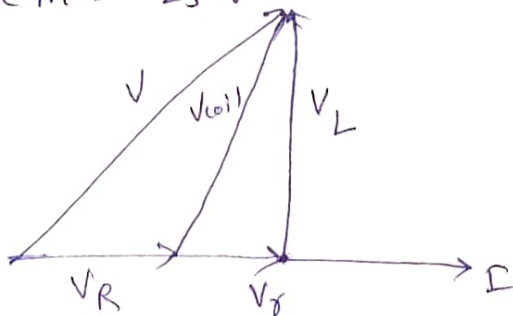

(2M)

Q. 3 A)

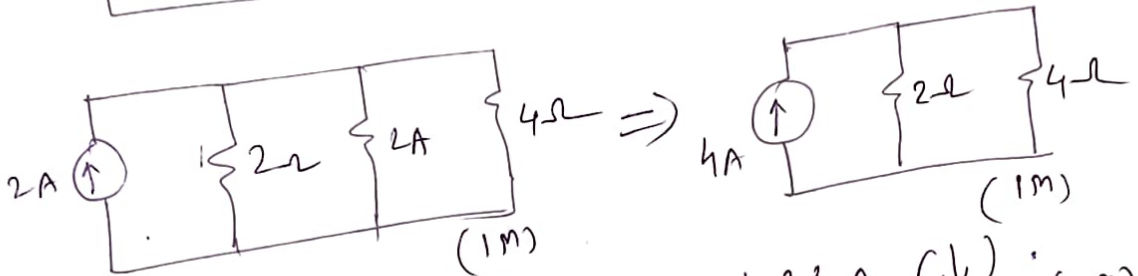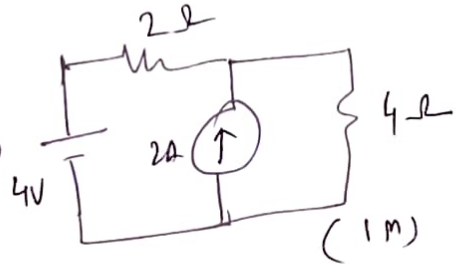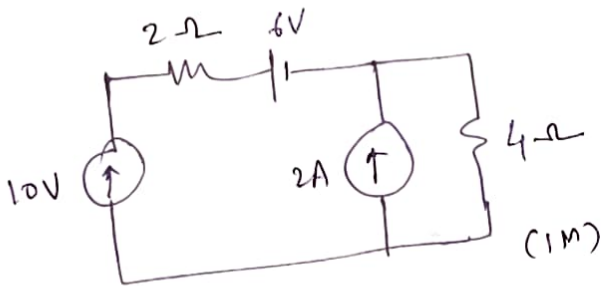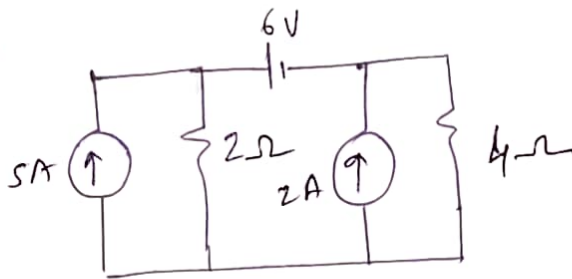

$$I_{4\Omega} = 4 \times \frac{2}{2+4} = 1.33 \text{ A } (\downarrow) \quad (1 \text{ M})$$

Q. 3 B) Zener diode as voltage regulator

2 MARKS

Figure

3 MARKS

Explanation

c) core type & shell type Transformer comparison.

5 valid pts - 5 M

(figures compulsory)

d) $V_1 = 25 \sin \omega t$

$V_2 = 10 \sin (\omega t + \pi/6)$

$V_3 = 30 \cos \omega t \Rightarrow 30 \sin (\omega t + \pi/2)$

$V_4 = 20 \sin (\omega t - \pi/4)$

(1 M)

converting into polar forms,

5

$$\bar{V}_1 = (17.68 \angle 0^\circ) V$$

$$\bar{V}_2 = (7.07 \angle 30^\circ) V$$

$$\bar{V}_3 = (21.21 \angle 90^\circ) V$$

$$\bar{V}_4 = (14.14 \angle -45^\circ) V$$

(1M)

polar to rectangular conversion,

$$\bar{V}_1 = (17.68 + j0) V$$

$$\bar{V}_2 = (6.12 + j3.54) V$$

$$\bar{V}_3 = (0 + j21.21) V$$

$$\bar{V}_4 = (10 - j10) V$$

(1M)

$$\bar{V} = \bar{V}_1 + \bar{V}_2 + \bar{V}_3 + \bar{V}_4$$

$$= (17.68 + j0) + (6.12 + j3.54) + (0 + j21.21) + (10 - j10)$$

$$= 33.8 + j14.75) V$$

(1M)

converting into polar form,

$$\bar{V} = (36.88 \angle 23.58^\circ) V$$

std. sinusoidal form,

$$v = 52.16 \sin(\omega t + 23.58^\circ)$$

(1M)